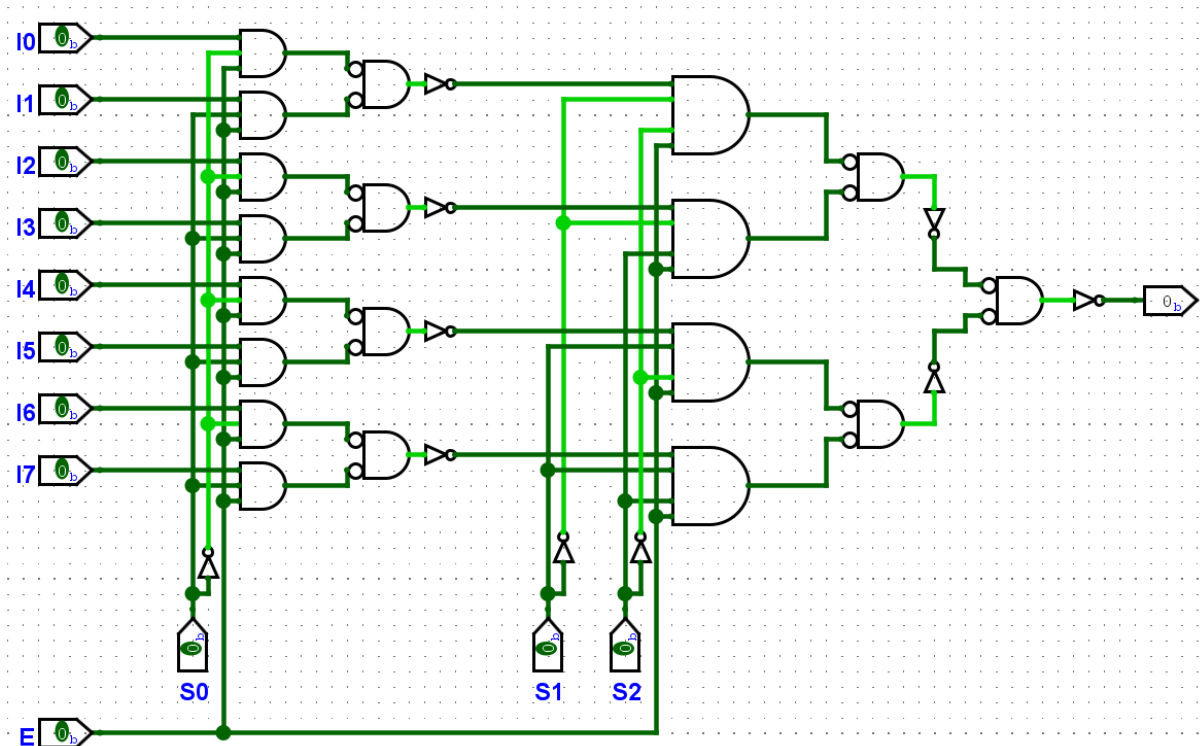


**Kode Asdos: RAI**[illegible]

B. 8-to-1 multiplexer dengan menggunakan AND gate, NOT gate, serta menggunakan enabler.



2. Buatlah masing-masing rangkaian berikut dengan menggunakan **4-to-1 line multiplexer**, dengan disertai tahapan *specification*, *formulation*, beserta *technology mapping*: (sertakan *screenshot* masing-masing rangkaian)

a. Rangkaian yang mengubah input **4-bit Binary Code** menjadi **4-bit Gray Code**.

### 1. Specification

- 4-bit Binary Code to 4-bit Gray Code
- Transforms Binary code to Gray Code
- 4-bit Binary code from 0 through 15: 4-bit patterns from 0000 to 1111, respectively.
- 4-bit Gray Code from 0 through 15: 4-bit patterns from 0000 to 1000, Gray code is an unweighted code
- Implementation:
  - Using 4-to-1 Line Multiplexers, OR gates, AND Gates, and NOT Gates
  - Multiple-level circuit

### 2. Formulations

- Conversions of any 4-bit code can be formulated by truth table
- Variables:
  - o Binary Code: A, B, C, D
  - o Gray Code: W, X, Y, Z

### Truth Table


Index	Input Binary Code				Gray Code			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

Optimization:

For a more simplified conversion, make a rudimentary function. For this case, D is used to be a rudimentary function for X, Y, and Z

Binary ABCD	Gray Code WXYZ	Rudimentary Function of D for X	Rudimentary Functions of D for Y	Rudimentary Functions of D for Z
0000	0000	F = 0	F = 0	F = D
0001	0001			
0010	0011	F = 0	F = 1	F = D'
0011	0010			
0100	0110	F = 1	F = 1	F = D
0101	0111			
0110	0101	F = 1	F = 0	F = D'
0111	0100			
1000	1100	F = 1	F = 0	F = D
1001	1101			
1010	1111	F = 1	F = 1	F = D'
1011	1110			
1100	1010	F = 0	F = 1	F = D
1101	1011			
1110	1001	F = 0	F = 0	F = D'
1111	1000			

### 3. Technology Mapping

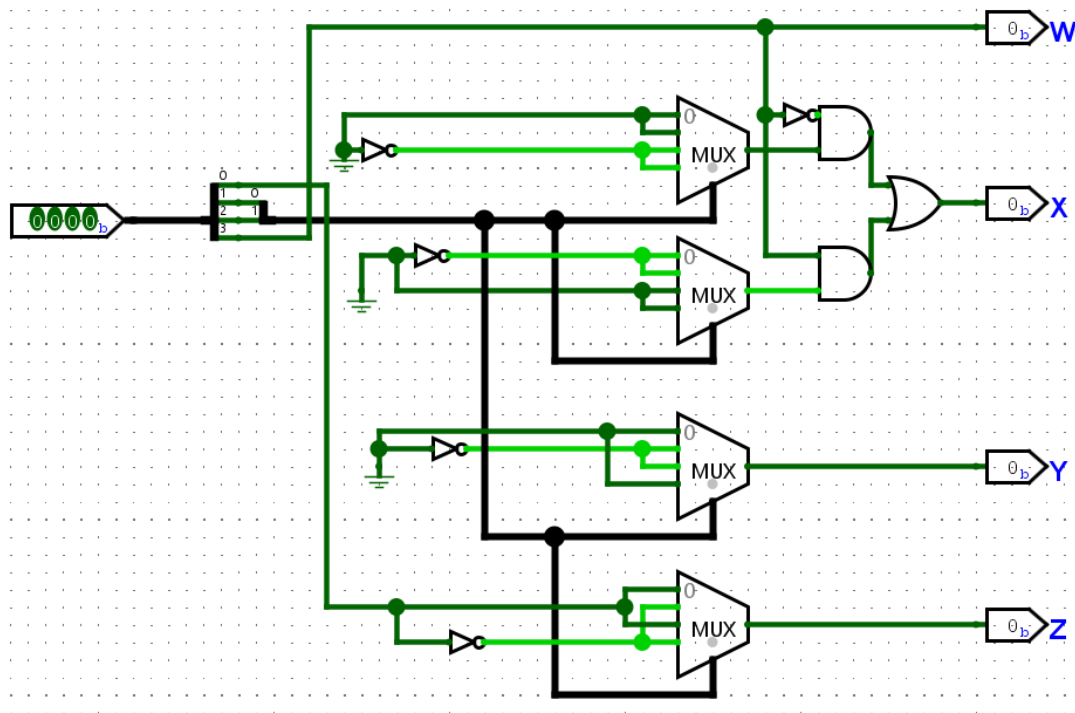

#### Truth Table

16 of 16 rows shown

$a[3..0]$	W	X	Y	Z
0 0 0 0	0	0	0	0
0 0 0 1	0	0	0	1
0 0 1 0	0	0	1	1
0 0 1 1	0	0	1	0
0 1 0 0	0	1	1	0
0 1 0 1	0	1	1	1
0 1 1 0	0	1	0	1
0 1 1 1	0	1	0	0
1 0 0 0	1	1	0	0
1 0 0 1	1	1	0	1
1 0 1 0	1	1	1	1
1 0 1 1	1	1	1	0
1 1 0 0	1	0	1	0
1 1 0 1	1	0	1	1
1 1 1 0	1	0	0	1
1 1 1 1	1	0	0	0

#### Note:

For Y and Z, only one 4-to-1 multiplexers that is needed and necessary because the rudimentary for  $A = 0$  and  $A = 1$  is exactly the same.

But for X, the rudimentary shows that  $A = 0$  isn't the same as  $A = 1$ . Therefore, gates such as OR, AND, and NOT gates are needed to make the functions work and suit the truth table.

**b. Rangkaian yang menerima 4-bit Binary Code kemudian mengubahnya menjadi 3-bit output XYZ, dengan masing-masing fungsi sebagai berikut:**

- $X(A, B, C, D) = \sum m(0, 1, 6, 7, 8, 9, 14, 15)$
- $Y(A, B, C, D) = \sum m(2, 3, 10, 11)$
- $Z(A, B, C, D) = \sum m(0, 2, 5, 7, 9, 11, 12, 14)$

1. Specification

- a. 4-bit Binary code to 3-bit output
- b. Transform 4-bit Binary code to 3-bit output as shown before in the functions.
- c. 4-bit Binary code from 0 through 15: 4-bit patterns from 0000 to 1111, respectively
- d. Implementation:
  - Using 4-to-1 Line Multiplexers, OR gates, AND Gates, and NOT Gates
  - Multiple-level circuit

2. Formulations

- Conversions of any 4-bit code can be formulated by truth table
- Variables:
  - a. Binary Code: A, B, C, D
  - b. 3-bit Output: X, Y, Z


Index	Input Binary Code				Output		
	A	B	C	D	X	Y	Z
0	0	0	0	0	1	0	1
1	0	0	0	1	1	0	0
2	0	0	1	0	0	1	1
3	0	0	1	1	0	1	0
4	0	1	0	0	0	0	0
5	0	1	0	1	0	0	1
6	0	1	1	0	1	0	0
7	0	1	1	1	1	0	1
8	1	0	0	0	1	0	0
9	1	0	0	1	1	0	1
10	1	0	1	0	0	1	0
11	1	0	1	1	0	1	1
12	1	1	0	0	0	0	1
13	1	1	0	1	0	0	0
14	1	1	1	0	1	0	1
15	1	1	1	1	1	0	0

Optimization:

For a more simplified conversion, make a rudimentary function. For this case, D is used to be a rudimentary function for X, Y, and Z

Binary ABCD	Output XYZ	Rudimentary Function of D for X	Rudimentary Functions of D for Y	Rudimentary Functions of D for Z
0000	101	F = 1	F = 0	F = D'
0001	100			
0010	011			
0011	010	F = 0	F = 1	F = D'
0100	000			
0101	001			
0110	100	F = 0	F = 0	F = D
0111	101			
1000	100			
1001	101	F = 1	F = 0	F = D
1010	010			
1011	011			
1100	001	F = 0	F = 0	F = D'
1101	000			
1110	101			
1111	100	F = 1	F = 0	F = D'

### 3. Technology Mapping

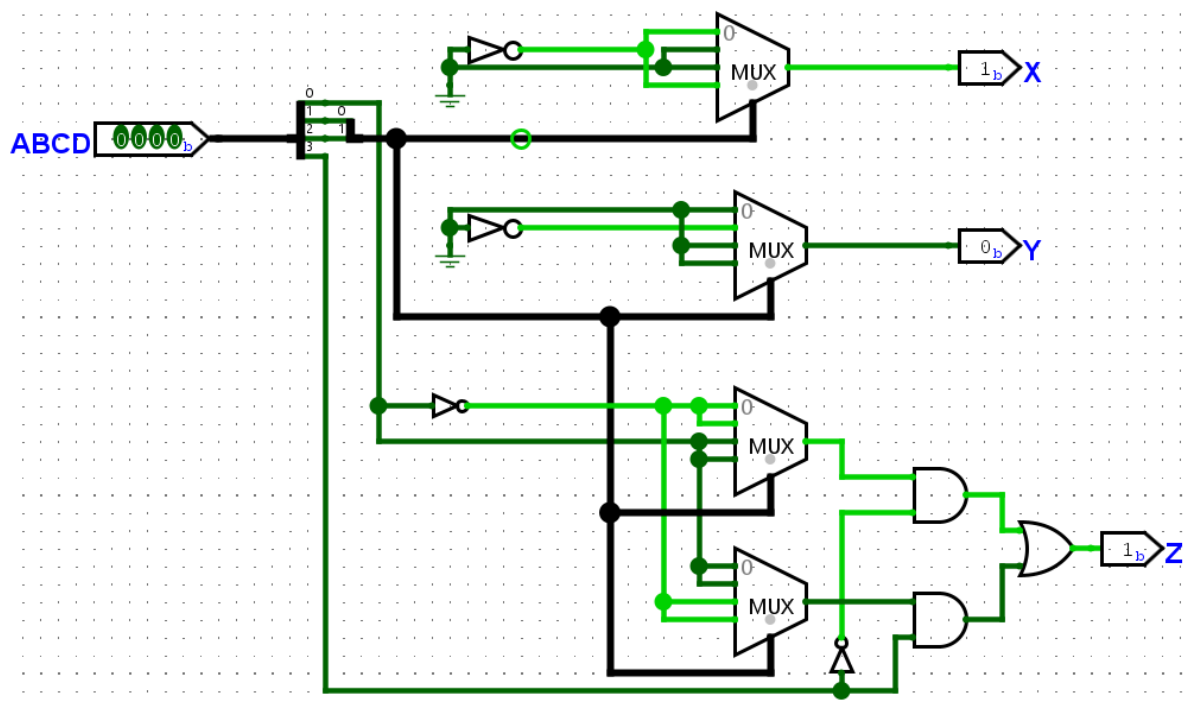

### Truth Table

16 of 16 rows shown

ABCD[3..0]	X	Y	Z
0 0 0 0	1	0	1
0 0 0 1	1	0	0
0 0 1 0	0	1	1
0 0 1 1	0	1	0
0 1 0 0	0	0	0
0 1 0 1	0	0	1
0 1 1 0	1	0	0
0 1 1 1	1	0	1
1 0 0 0	1	0	0
1 0 0 1	1	0	1
1 0 1 0	0	1	0
1 0 1 1	0	1	1
1 1 0 0	0	0	1
1 1 0 1	0	0	0
1 1 1 0	1	0	1
1 1 1 1	1	0	0

### Note:

For X and Y, only one 4-to-1 multiplexers that is needed and necessary because the rudimentary for A = 0 and A = 1 is exactly the same.

But for Z, the rudimentary shows that A = 0 isn't the same as A = 1. Therefore, gates such as OR, AND, and NOT gates are needed to make the functions work and suit the truth table.

3. Lakukan tahapan *formulation*, *optimization*, dan *technology mapping* untuk masing-masing fungsi berikut: (sertakan *screenshot* masing-masing rangkaian)
- a.  $F(A, B, C, D) = \sum m(0, 2, 8, 9, 10, 14)$ ,  
 $d(A, B, C, D) = \sum m(1, 4, 5, 7, 15)$

### Formulation

Truth Table

Index	A	B	C	D	F
0	0	0	0	0	1
1	0	0	0	1	X
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	X
5	0	1	0	1	X
6	0	1	1	0	0
7	0	1	1	1	X
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	X

### Optimization


Making the K-Map for optimizing the functions

	C'		C		
A'	1 0	X 1	0 3	1 2	B'
	X 4	X 5	X 7	0 6	B
A	0 12	0 13	X 15	1 14	
	1 8	1 9	0 11	1 10	B'
	D'	D		D'	

Optimized functions will be:

$$F = B'D' + B'C' + ACD'$$

### Technology Mapping

 

### Truth Table

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$$F = \overline{B} \cdot \overline{D} + \overline{B} \cdot C + A \cdot C \cdot \overline{D}$$



- b.  $F(A, B, C, D) = \prod M(3, 4, 5, 7, 8, 10, 11)$   
 $d(A, B, C, D) = \sum m(1, 2, 6, 9, 15)$

### Formulation

Truth Table

Index	A	B	C	D	F
0	0	0	0	0	1
1	0	0	0	1	X
2	0	0	1	0	X
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	X
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	X
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	X

### Optimization


Making the K-Map for optimizing the functions

	C		C'		
A	1      0	X      1	0      3	X      2	B
	0      4	0      5	0      7	X      6	B'
A'	1      12	1      13	X      15	1      14	
	0      8	X      9	0      11	0      10	B
	D		D'		

Optimized functions will be:

$$F = (A+B').(A'+B).(C'+D')$$

## Technology Mapping

 

## Truth Table

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$F = (\overline{A+B}) \cdot (\overline{A+B}) \cdot (\overline{C+D})$$

Link to author's Logisim file: [Link to Logisim \(Google drive\)](#)

😊 PSD IS FUN 😊